

# Template Week 3 – Hardware

Student number: 589531

## Assignment 3.1: Examine your phone

What processor is in your phone?

**Apple A15 Bionic chip.**

To which architecture family does this processor belong? In other words, which Instruction Set Architecture (ISA) is used?

**ARM-architectuur, specifiek ARMv8-A**

How much RAM is in it?

**6 GB ram**

How much storage does your phone have?

**128GB**

What operating system is running on your phone?

**IOS 26.1**

Approximately how many applications do you have installed?

**112**

Which application do you use the most?

**YouTube**

Can your phone be charged with what type of plug?

**Lightning-kabel**

Which I/O ports can you visually see on your phone?

**Lightning kabel**

**SIM-Kaart**

**Luidspreker en microfoon punten**

### **Assignment 3.2: Examine your laptop**

What processor is in your laptop?

**I5-8250U**

To which architecture family does this processor belong? In other words, which Instruction Set Architecture (ISA) is used?

**X86-64**

How much RAM is in it?

**16GB**

How much storage does your laptop have?

**1tb HDD – 128GB SSD**

Which operating system is running on your laptop?

**Win 11**

Approximately how many applications do you have installed?

**150 ish**

Which application do you use the most?

**Google Chrome**

Can your laptop be charged with what type of plug?

**Netadapter**

Which I/O ports can you visually see on your laptop?

**1 x USB-C**

**2 x USB-A**

**1 x HDMI**

**1 x 3,5mm audio jack**

**1 x SD kaartlezer**

**1 x oplaad poort**

**1 x Ethernet poort**

### **Assignment 3.3: Power to the laptop**

What is the input voltage?

**100-240v**

What is the output voltage?

**19,5V**

How many watts can your power adapter deliver?

**45W**

Is the input voltage AC or DC?

**AC**

Is the output voltage AC or DC?

**DC**

AC/DC what is that?

**AC = Stroom wisselt hele tijd van richting.,**

**DC = Stroom gaat maar een richting op.**

If you reverse the polarity of the output voltage, is that bad for your laptop?


**Ja dan word de binnen kant gefrituurd.**


You forgot your power adapter, your laptop normally needs 15 watts. You will be loaned a power adapter that can deliver 50 watts. Voltage, polarity, etc. are all the same compared to the original power adapter. You can connect the borrowed power adapter to your laptop. What will happen? Also explain why you think that.


Er gaat niks raars gebeuren de laptop pakt alleen de stroom die die nodig heeft en niet meer.

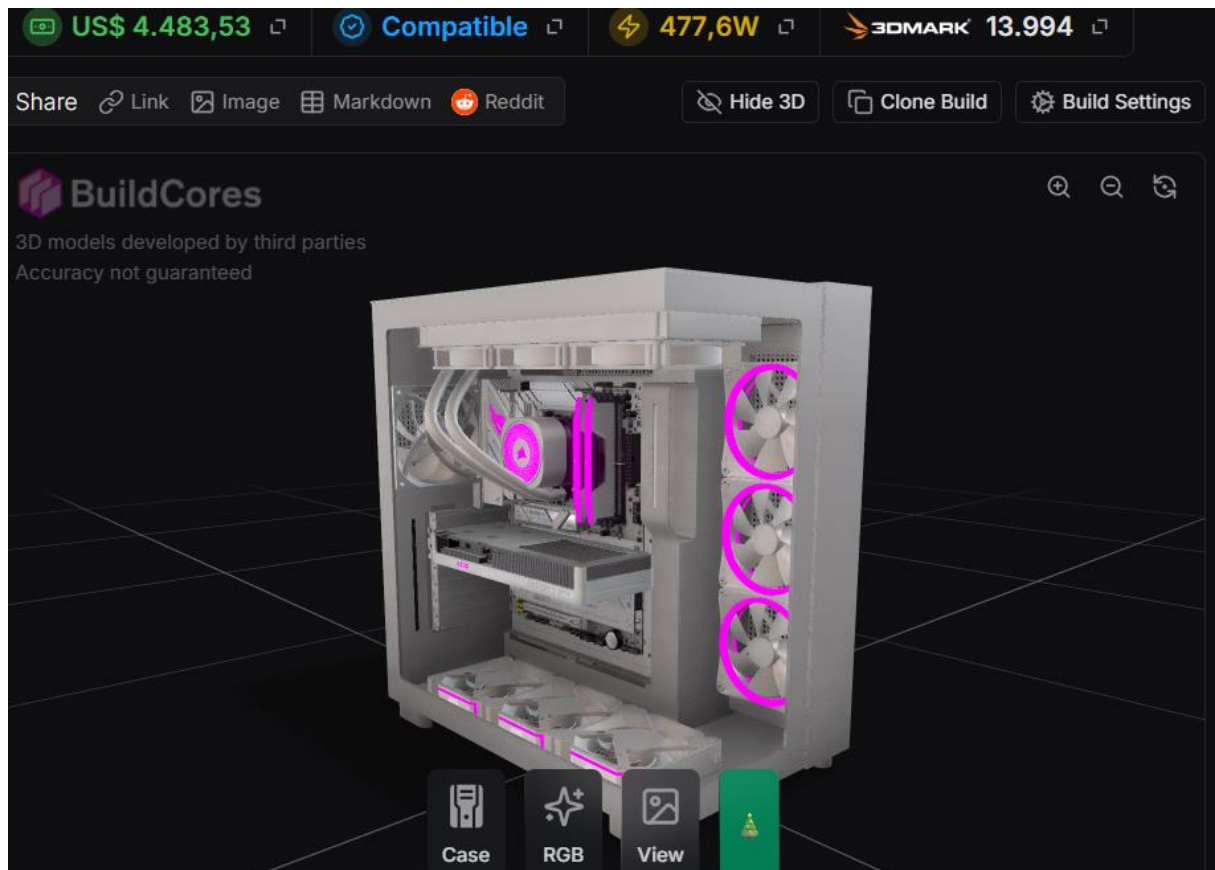
### **Assignment 3.4: Build your dream PC**



Screenshots PC configuration + motivation:




 Parts List

 Price History

 Case






\$249.99





Walmart


Buy



 CPU






\$675.59





amazon


Buy



 Motherboard






\$239.99





Walmart


Buy



 GPU






\$322.99



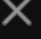


amazon

Buy




 Add

 RAM






\$1,110.99

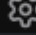




CORSAIR

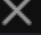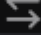Buy




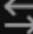

 Add



 CPU Cooler  Configure




Corsair NAUTILUS Water 360mm RS ARGB 74.37 CFM White


\$119.99 

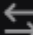

amazon [Buy](#)  


 Storage  Add




Samsung 990 EVO 2TB SSD M.2-2280 PCIe 5.0 X2 NVMe


\$209.99 




BEST BUY [Buy](#)  




 Power Supply




Lian Li EDGE White 850W Fully Modular 80+ Gold


\$139.00 



Walmart  [Buy](#)  



 Case Fan  Configure  Add




darkFlash INF34 ARGB PWM 120mm White 3-Pack

\$37.06 

amazon [Buy](#)  

 Monitor  Add




Dell Alienware AW3425DW 34.2" 1440p 240Hz QD-OLED Curved Monitor

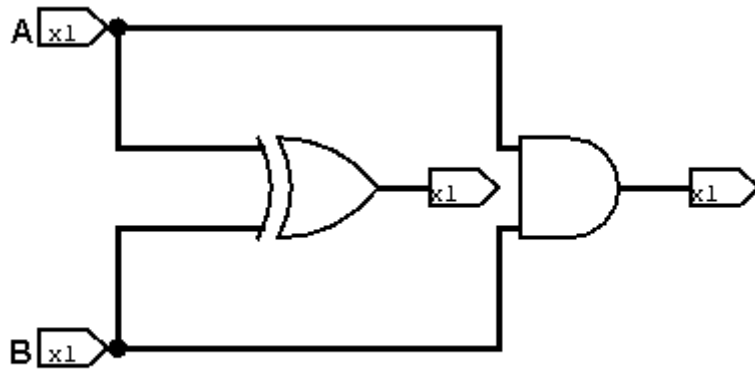
### Assignment 3.5: Adders

Complete the **half adder**, **full adder** and **4-bit adder** assignment as described in the PowerPoint slides of week 3 in Logisim. Save the chip design and also export three PNG pictures of the separate finished designs. See the PowerPoint slides of week 3.


Paste the three exported PNG pictures in here.



Ayoub Youssoufi 589531

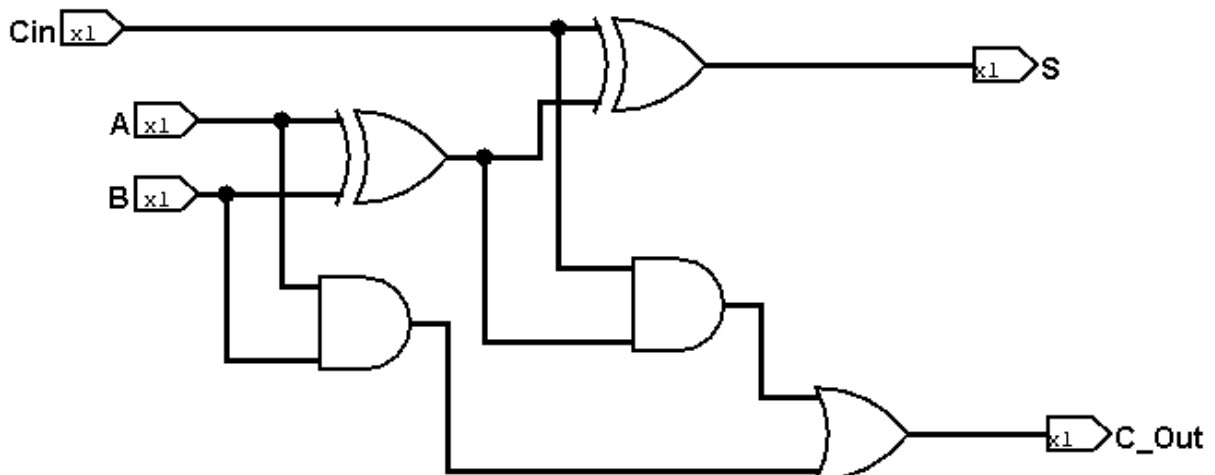

Ayoub Youssoufi 589531

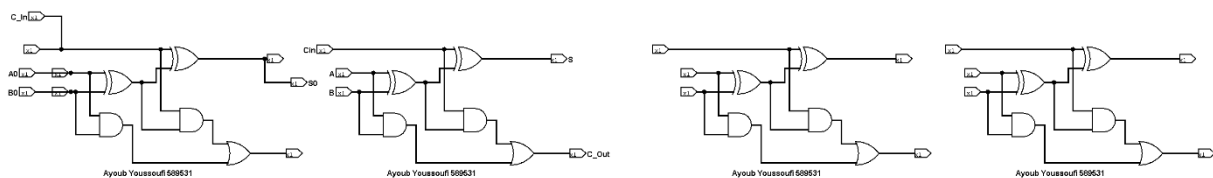

A1 [ ] B1 [ ]  
A2 [ ] B2 [ ]  
A3 [ ] B3 [ ]

S1  
S2  
S3

Ready? Save this file and export it as a pdf file with the name: [week3.pdf](#)